

EE6503 POWER ELECTRONICS

AC VOLTAGE CONTROLLERS

1. Introduction.

AC voltage controllers (ac line voltage controllers) are employed to vary the RMS value of the alternating voltage applied to a load circuit. An ac voltage controller is a type of thyristor power converter which is used to convert a fixed voltage, fixed frequency ac input supply to obtain a variable voltage ac output. The RMS value of the ac output voltage and the ac power flow to the load is controlled by varying (adjusting) the trigger angle ' α '

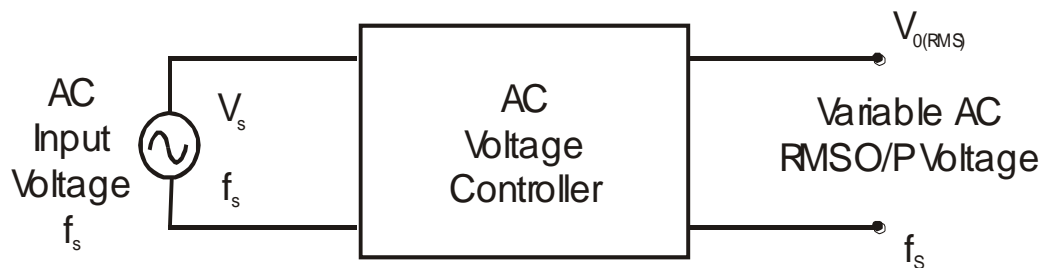


Fig.1

2. TYPE OF AC VOLTAGE CONTROLLERS

The ac voltage controllers are classified into two types based on the type of input ac supply applied to the circuit.

- Single Phase AC Controllers.
- Three Phase AC Controllers.

Single phase ac controllers operate with single phase ac supply voltage of 230V RMS at 50Hz in our country. Three phase ac controllers operate with 3 phase ac supply of 400V RMS at 50Hz supply frequency.

Each type of controller may be sub divided into

- Uni-directional or half wave ac controller.
- Bi-directional or full wave ac controller.

In brief different types of ac voltage controllers are

- Single phase half wave ac voltage controller (uni-directional controller).
- Single phase full wave ac voltage controller (bi-directional controller).

- Three phase half wave ac voltage controller (uni-directional controller).
- Three phase full wave ac voltage controller (bi-directional controller).

3. APPLICATIONS OF AC VOLTAGE CONTROLLERS

- Lighting / Illumination control in ac power circuits.
- Induction heating.
- Industrial heating & Domestic heating.
- Transformers tap changing (on load transformer tap changing).
- Speed control of induction motors (single phase and poly phase ac induction motor control).
- AC magnet controls.

4. AC VOLTAGE CONTROL TECHNIQUES

There are two different types of thyristor control used in practice to control the ac power flow

1. Phase control
2. On-Off control

These are the two ac output voltage control techniques.

In On-Off control technique Thyristors are used as switches to connect the load circuit to the ac supply (source) for a few cycles of the input ac supply and then to disconnect it for few input cycles. The Thyristors thus act as a high speed contactor (or high speed ac switch).

4.1 PHASE CONTROL TECHNIQUE

In phase control the Thyristors are used as switches to connect the load circuit to the input ac supply, for a part of every input cycle. That is the ac supply voltage is chopped using Thyristors during a part of each input cycle.

The thyristor switch is turned on for a part of every half cycle, so that input supply voltage appears across the load and then turned off during the remaining part of input half cycle to disconnect the ac supply from the load.


By controlling the phase angle or the trigger angle ' α ' (delay angle), the output RMS voltage across the load can be controlled.

The trigger delay angle ' α ' is defined as the phase angle (the value of ωt) at which the thyristor turns on and the load current begins to flow.

SINGLE PHASE FULL WAVE AC VOLTAGE CONTROLLER (AC REGULATOR) OR RMS VOLTAGE CONTROLLER WITH RESISTIVE LOAD

A single phase full wave ac voltage controller with a resistive load is shown in the figure below. It is possible to control the ac power flow to the load in both the half cycles by adjusting the trigger angle ' α '. Hence the full wave ac voltage controller is also referred to as a bidirectional controller.

Circuit Diagram:

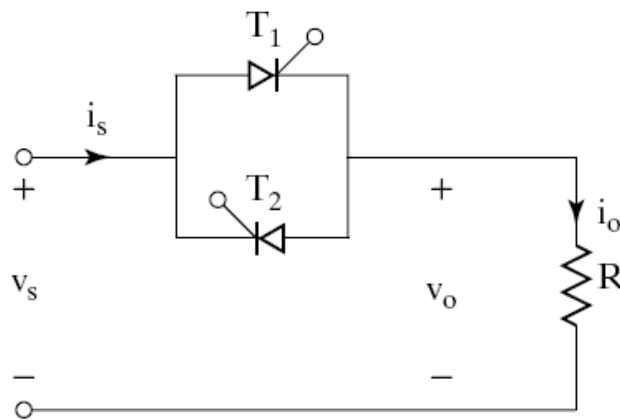

OPERATION

Mode-1- From 0 to π

The thyristor T1 is forward biased during the positive half cycle of the input supply voltage. The thyristor T1 is triggered at a delay angle of α ($0 \leq \alpha \leq \pi$). Considering the ON thyristor T1 as an ideal closed switch the input supply voltage appears across the load resistor R_L and the output voltage $v_o = v_s$.


During $\omega t = \alpha$ to π radians. The load current flows through the ON thyristor T1 and through the load resistor R_L in the downward direction during the conduction time of T1 from $\omega t = \alpha$ to π radians

Mode-2- From π to 2π

At $\omega t = \pi$, when the input voltage falls to zero the thyristor current (which is flowing through the load resistor R_L) falls to zero and hence T1 naturally turns off. No current flows in the circuit during $\omega t = \pi$ to $(\pi + \alpha)$. The thyristor T2 is forward biased

during the negative cycle of input supply and when thyristor T2 is triggered at a delay angle $(\pi + \alpha)$, the output voltage follows the negative halfcycle of input from $\omega t = (\pi + \alpha)$ to 2π . When T2 is ON, the load current flows in the reverse direction (upward direction) through T2 during $\omega t = (\pi + \alpha)$ to 2π radians. The time interval (spacing) between the gate trigger pulses of T1 and T2 is kept at π radians or 180°. At $\omega t = 2\pi$, the input supply voltage falls to zero and hence the load current also falls to zero and thyristor T2 turn off naturally.

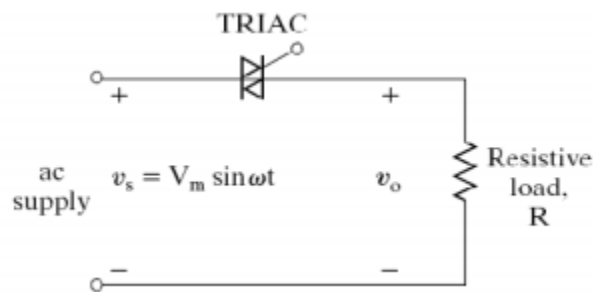
Instead of using two SCR's in parallel, a Triac can be used for full wave ac voltage control. For applications up to 400Hz,.



Phase control Thyristors which are relatively inexpensive, converter grade Thyristors which are slower than fast switching inverter grade Thyristors are normally used.

Due to ac line commutation or natural commutation, there is no need of extra commutation circuitry or components and the circuits for ac voltage controllers are very simple.

WAVEFORMS

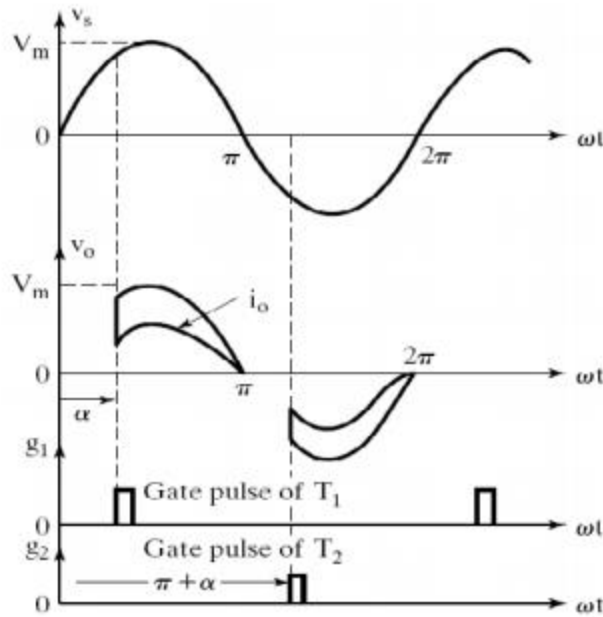


g: Waveforms of single phase full wave ac voltage controller

SINGLE PHASE FULL WAVE AC VOLTAGE CONTROLLER (BIDIRECTIONAL CONTROLLER) WITH RL LOAD

if we consider a single phase full wave ac voltage controller controlling the speed of a single phase ac induction motor, the load which is the induction motor winding is an RL type of load, where R represents the motor winding resistance and L represents the motor winding inductance.

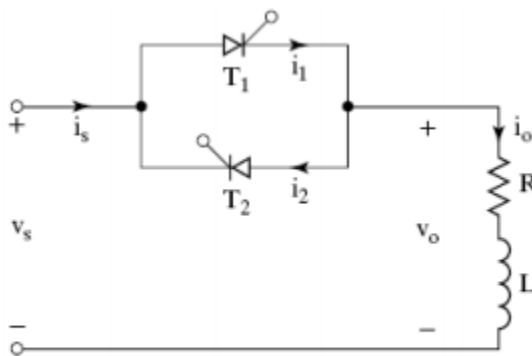A single phase full wave ac voltage controller circuit (bidirectional controller) with an RL load using two thyristors T1 and T2 (T1 and T2 are two SCRs) connected in parallel is shown below.



; Single phase full wave ac voltage controller with RL load

The thyristor T1 is forward biased during the positive half cycle of input supply. Let us assume that T1 is triggered at $\omega\alpha t = \alpha$, by applying a suitable gate trigger pulse to T1 during the positive half cycle of input supply. The output voltage across the load follows the input supply voltage when T1 is ON. The load current i_o flows through the thyristor T1 and through the load

in the downward direction. This load current pulse flowing through T1 can be considered as the positive current pulse. Due to the inductance in the load, the load current is flowing through T1 would not fall to zero at $\omega t = \pi$, when the input supply voltage starts to become negative. The thyristor T1 will continue to conduct the load current until all the inductive energy stored in the load inductor L is completely utilized and the load current through T1 falls to zero at $\omega t = \beta$, where β is referred to as the Extinction angle, (the value of ωt) at which the load current falls to zero. The extinction angle β is measured from the point of the beginning of the positive half cycle of input supply to the point where the load current falls to zero. The thyristor T1 conducts from $\omega t = \alpha$ to β . The conduction angle of T1 is $\delta = (\beta - \alpha)$, which depends on the delay angle α and the load impedance angle ϕ . The waveforms of the input supply voltage, the gate trigger pulses of T1 and T2, the thyristor current, the load current and the load voltage waveforms appear as shown in the figure below.

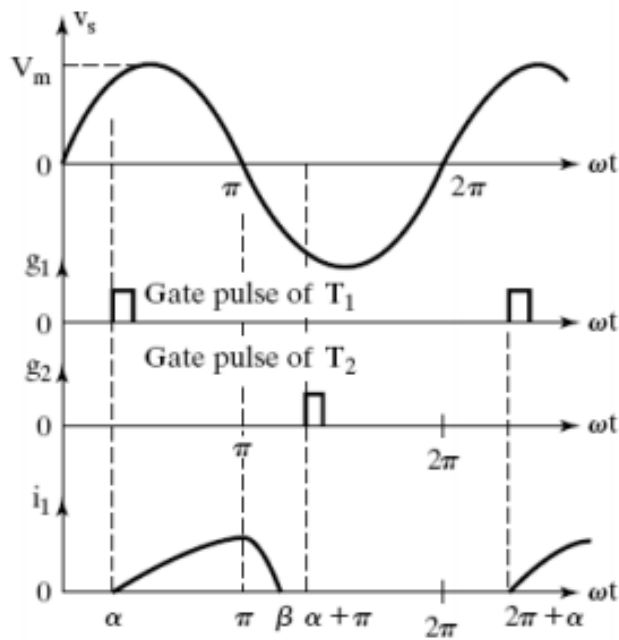


Fig. 1: Input supply voltage & Thyristor current waveforms

Waveforms of single phase full wave ac voltage controller with RL load for $\alpha > \phi$. Discontinuous load current operation occurs for $\alpha > \phi$ and $\beta < (\pi + \alpha)$; i.e., $(\beta - \alpha) < \pi$, conduction angle $< \pi$.


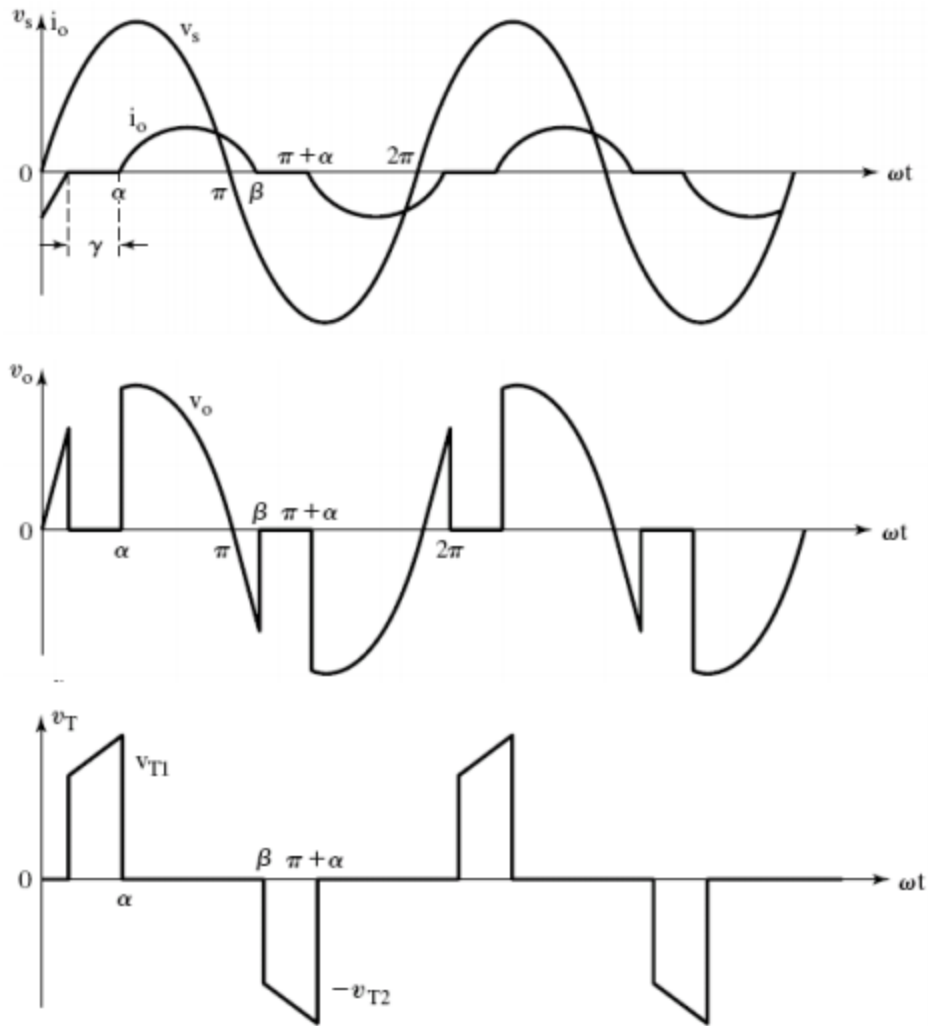


Fig.: Waveforms of Input supply voltage, Load Current, Load Voltage and Thyristor Voltage across T_1

- The RMS value of the output voltage and the load current may be varied by varying the trigger angle α .
- This circuit, AC RMS voltage controller can be used to regulate the RMS voltage across the terminals of an ac motor (induction motor). It can be used to control the temperature of a furnace by varying the RMS output voltage.
- For very large load inductance 'L' the SCR may fail to commute, after it is triggered and the load voltage will be a full sine wave (similar to the applied input supply voltage and the output control will be lost) as long as the gating signals are applied to the thyristors T_1 and T_2 . The load current waveform will appear as a full continuous sine wave and the load current waveform lags behind the output sine wave by the load power factor angle ϕ .

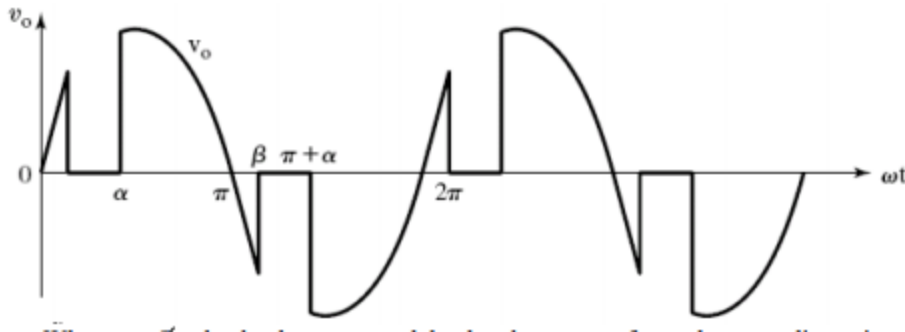TO DERIVE AN EXPRESSION FOR RMS OUTPUT VOLTAGE V_o OF A SINGLE PHASE FULL-WAVE AC VOLTAGE CONTROLLER WITH RL LOAD.



$$V_{o(RMS)} = \left[\frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t d(\omega t) \right]^{\frac{1}{2}}$$

Output $v_o = V_m \sin \omega t$, for $\omega t = \alpha$ to β , when T_1 is ON.

$$V_{o(RMS)} = \left[\frac{V_m^2}{\pi} \int_{\alpha}^{\beta} \frac{(1 - \cos 2\omega t)}{2} d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{o(RMS)} = \left[\frac{V_m^2}{2\pi} \left\{ \int_{\alpha}^{\beta} d(\omega t) - \int_{\alpha}^{\beta} \cos 2\omega t d(\omega t) \right\} \right]^{\frac{1}{2}}$$

$$V_{o(RMS)} = \left[\frac{V_m^2}{2\pi} \left\{ (\omega t) \Big|_{\alpha}^{\beta} - \left(\frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{\beta} \right\} \right]^{\frac{1}{2}}$$

$$V_{o(RMS)} = \left[\frac{V_m^2}{2\pi} \left\{ (\beta - \alpha) - \frac{\sin 2\beta}{2} + \frac{\sin 2\alpha}{2} \right\} \right]^{\frac{1}{2}}$$

$$V_{o(RMS)} = V_m \left[\frac{1}{2\pi} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right\} \right]^{\frac{1}{2}}$$

$$V_{o(RMS)} = \frac{V_m}{\sqrt{2}} \left[\frac{1}{\pi} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right\} \right]^{\frac{1}{2}}$$


The RMS output voltage across the load can be varied by changing the trigger angle α . For a purely resistive load $L = 0$, therefore load power factor angle $\phi = 0$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = 0 ;$$

Extinction angle $\beta = \pi$ radians = 180°

4.2 PRINCIPLE OF ON-OFF CONTROL TECHNIQUE (INTEGRAL CYCLE CONTROL)

Circuit Diagram:

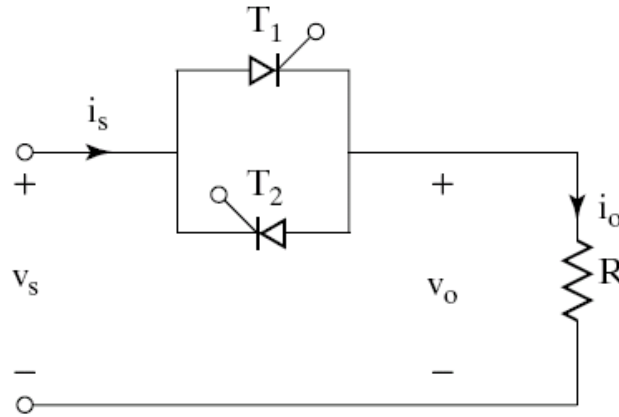

$$R = R_L = \text{Load Resistance}$$

Fig.2: Single phase full wave AC voltage controller circuit

The basic principle of on-off control technique is explained with reference to a single phase full wave ac voltage controller circuit shown below. The thyristor switches T_1 and T_2 are turned on by applying appropriate gate trigger pulses to connect the input ac supply to the load for 'n' number of input cycles during the time interval t_{ON} . The thyristor switches T_1 and T_2 are turned off by blocking the gate trigger pulses for 'm' number of input cycles during the time interval t_{OFF} . The ac controller ON time t_{ON} usually consists of an integral number of input cycles.

Waveforms:

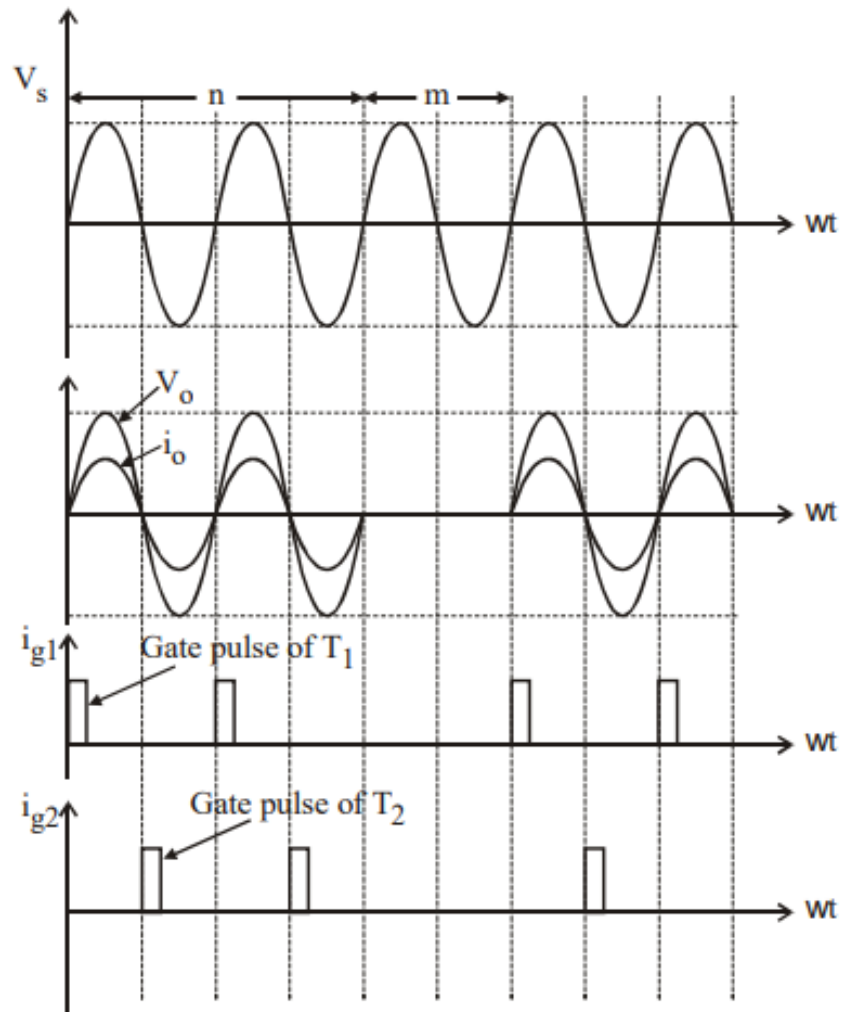


Fig.: Waveforms

Example

Referring to the waveforms of ON-OFF control technique in the above diagram,

n = Two input cycles. Thyristors are turned ON during t_{ON} for two input cycles.

m = One input cycle. Thyristors are turned OFF during t_{OFF} for one input cycle

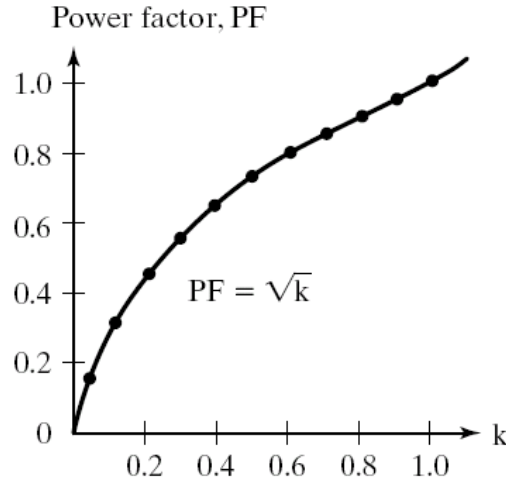


Fig.4: Power Factor

Operation:

Thyristors are turned ON precisely at the zero voltage crossings of the input supply.

Mode-1

The thyristor T_1 is turned on at the beginning of each positive half cycle by applying the gate trigger pulses to T_1 as shown, during the ON time t_{ON} . The load current flows in the positive direction, which is the downward direction as shown in the circuit diagram when T_1 conducts.

Mode-1

The thyristor T_2 is turned on at the beginning of each negative half cycle, by applying gating signal to the gate of T_2 , during t_{ON} . The load current flows in the reverse direction, which is the upward direction when T_2 conducts. Thus we obtain a bi-directional load current flow (alternating load current flow) in a ac voltage controller circuit, by triggering the thyristors alternately.

This type of control is used in applications which have high mechanical inertia and high thermal time constant (Industrial heating and speed control of ac motors). Due to zero voltage and zero current switching of Thyristors, the harmonics generated by switching actions are reduced.

For a sine wave input supply voltage,

$$v_s = V_m \sin \omega t = \sqrt{2}V_s \sin \omega t$$

$$V_s = \text{RMS value of input ac supply} = \frac{V_m}{\sqrt{2}} = \text{RMS phase supply voltage.}$$

If the input ac supply is connected to load for 'n' number of input cycles and disconnected for 'm' number of input cycles, then

$$t_{ON} = n \times T, \quad t_{OFF} = m \times T$$

Where $T = \frac{1}{f}$ = input cycle time (time period) and

f = input supply frequency.

t_{ON} = controller on time = $n \times T$.

t_{OFF} = controller off time = $m \times T$.

T_o = Output time period = $(t_{ON} + t_{OFF}) = (nT + mT)$.

We can show that,

$$\text{Output RMS voltage } V_{O(RMS)} = V_{i(RMS)} \sqrt{\frac{t_{ON}}{T_o}} = V_s \sqrt{\frac{t_{ON}}{T_o}}$$

Where $V_{i(RMS)}$ is the RMS input supply voltage = V_s .

5. Derivation

- RMS Output (Load) Voltage**

$$V_{O(RMS)} = \left[\frac{n}{2\pi(n+m)} \int_0^{2\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{n}{(m+n)}} = V_{i(RMS)} \sqrt{k} = V_s \sqrt{k}$$

$$V_{O(RMS)} = V_{i(RMS)} \sqrt{k} = V_s \sqrt{k}$$

Where $V_s = V_{i(RMS)}$ = RMS value of input supply voltage.

- **Duty Cycle**

$$k = \frac{t_{ON}}{T_o} = \frac{t_{ON}}{(t_{ON} + t_{OFF})} = \frac{nT}{(m+n)T}$$

Where, $k = \frac{n}{(m+n)}$ = duty cycle (d).

- **RMS Load Current**

$$I_{O(RMS)} = \frac{V_{O(RMS)}}{Z} = \frac{V_{O(RMS)}}{R_L}; \quad \text{for a resistive load } Z = R_L.$$

- **Output AC (Load) Power**

$$P_o = I_{O(RMS)}^2 \times R_L$$

- **Input Power Factor**

$$PF = \frac{P_o}{VA} = \frac{\text{output load power}}{\text{input supply volt amperes}} = \frac{P_o}{V_s I_s}$$

$$PF = \frac{I_{O(RMS)}^2 \times R_L}{V_{i(RMS)} \times I_{in(RMS)}}; \quad I_s = I_{in(RMS)} = \text{RMS input supply current.}$$

The input supply current is same as the load current $I_{in} = I_o = I_L$


Hence, RMS supply current = RMS load current; $I_{in(RMS)} = I_{O(RMS)}$.

$$PF = \frac{I_{O(RMS)}^2 \times R_L}{V_{i(RMS)} \times I_{in(RMS)}} = \frac{V_{O(RMS)}}{V_{i(RMS)}} = \frac{V_{i(RMS)} \sqrt{k}}{V_{i(RMS)}} = \sqrt{k}$$

$$PF = \sqrt{k} = \sqrt{\frac{n}{m+n}}$$

- **The Average Current of Thyristor $I_{T(Avg)}$**

Waveform of Thyristor Current

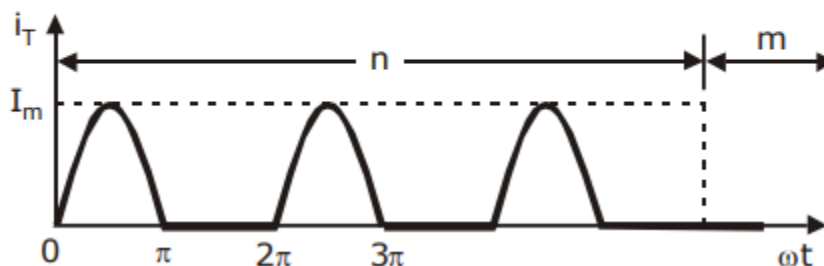

$$I_{T(Avg)} = \frac{n}{2\pi(m+n)} \int_0^\pi I_m \sin \omega t . d(\omega t)$$

$$I_{T(Avg)} = \frac{nI_m}{2\pi(m+n)} \int_0^\pi \sin \omega t . d(\omega t)$$

$$I_{T(Avg)} = \frac{nI_m}{2\pi(m+n)} \left[-\cos \omega t \Big/ \Big|_0^\pi \right]$$

$$I_{T(Avg)} = \frac{nI_m}{2\pi(m+n)} [-\cos \pi + \cos 0]$$

$$I_{T(Avg)} = \frac{nI_m}{2\pi(m+n)} [-(-1) + 1]$$

$$I_{T(Avg)} = \frac{n}{2\pi(m+n)} [2I_m]$$

$$I_{T(Avg)} = \frac{I_m n}{\pi(m+n)} = \frac{k.I_m}{\pi}$$

$$k = \text{duty cycle} = \frac{t_{ON}}{(t_{ON} + t_{OFF})} = \frac{n}{(n+m)}$$

$$I_{T(Avg)} = \frac{I_m n}{\pi(m+n)} = \frac{k.I_m}{\pi},$$

• **RMS Current of Thyristor** $I_{T(RMS)}$

$$I_{T(RMS)} = \left[\frac{n}{2\pi(n+m)} \int_0^\pi I_m^2 \sin^2 \omega t . d(\omega t) \right]^{1/2}$$

$$I_{T(RMS)} = \left[\frac{nI_m^2}{2\pi(n+m)} \int_0^\pi \sin^2 \omega t . d(\omega t) \right]^{1/2}$$

$$I_{T(RMS)} = \left[\frac{nI_m^2}{4\pi(n+m)} \left\{ (\pi - 0) - \left(\frac{\sin 2\pi - \sin 0}{2} \right) \right\} \right]^{1/2}$$

$$I_{T(RMS)} = \frac{I_m}{2} \sqrt{\frac{n}{m+n}} = \frac{I_m}{2} \sqrt{k}$$

$$I_{T(RMS)} = \frac{I_m}{2} \sqrt{k}$$

PROBLEM

1. A single phase full wave ac voltage controller working on ON-OFF control technique has supply voltage of 230V, RMS 50Hz, load = 50Ω. The controller is ON for 30 cycles and off for 40 cycles. Calculate

- ON & OFF time intervals.
- RMS output voltage.
- Input P.F.
- Average and RMS thyristor currents.

5. Conclusion:


Thyristor based ac voltage controllers have high efficiency, flexibility in control and require less maintenance. The disadvantage of ac voltage controllers is the introduction of harmonics in the supply current and load voltage waveforms particularly at low output voltage levels.

Power Factor Control

Power factor control, also known as correction of power factor, is the process of reducing the amount of reactive power. The power electronic device used in this case is called a power factor controller (PFC). From the power triangle (which comprises reactive, true and apparent power), the reactive power is at right angle (90°) to the true power and is used to energize the magnetic field. Although reactive power does not have a real value in electronic equipment, the bill for electricity comprises real and reactive power costs. This makes it necessary to have power factor controllers in electronic devices.

Power factor (k) is defined as the ratio of the real power (in kW) to the reactive power (in kVAr). Its value ranges from 0 to 1. If a device has a power factor of 0.8 and above, it is said to be using power efficiently. Incorporating a PFC ensures the power factor ranges from 0.95 to 0.99. Power factor controllers are mainly in industrial equipment to minimize reactive power generated by fluorescent lighting and electric motors.

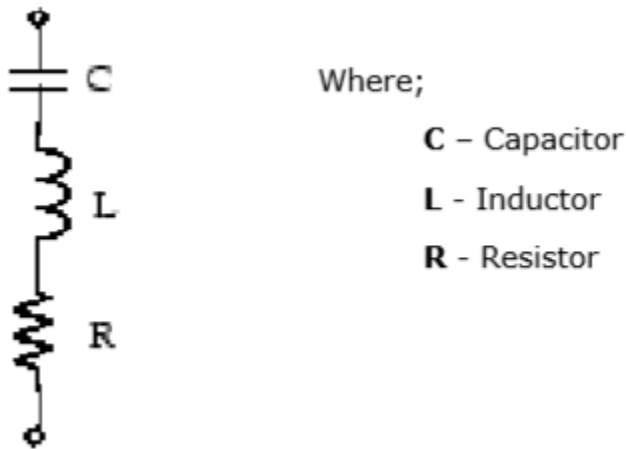To ensure power factor is improved without causing harmonic distortion, the conventional capacitors should not be used. Instead, filters (combination of capacitors and reactors) for harmonic suppression are used. The figure below shows a harmonic filter.



The above type of harmonic filter is referred to as a single tuned filter. A quality factor Q of this filter is defined as quality factor of its reactance (X_L) at Q (tuning frequency) where Q is given by (nX_L/R) .

Multistage sequence control

When two or more sequence control stages are connected, it is possible to have an improvement in power factor and further reduction in THD (total harmonic distortion). An n -stage sequence

control converter has n windings in the transformer secondary part with each rated e_s/n (the source voltage).

When two AC converters are placed parallel to each other, the zero sequence way is created. A little difference between the two converters causes a great zero sequence in circulating current. The diagram below shows the parallel system of a converter. The direction of the current is anti-clockwise with respect to that of the voltage system.

A cycloconverter refers to a frequency changer that can to change AC power from one frequency to AC power at another frequency. This process is known as AC-AC conversion. It is mainly used in electric traction, AC motors having variable speed and induction heating.

A cycloconverter can achieve frequency conversion in one stage and ensures that voltage and the frequencies are controllable. In addition, the need to use commutation circuits is not necessary because it utilizes natural commutation. Power transfer within a cycloconverter occurs in two directions (bidirectional).

A major problem with cycloconverters is that when it is operating at small currents, there are inefficiencies created with firing delay. Furthermore, operations are only smooth at frequencies that are not equal half frequency input values. This is true because a cycloconverter is an AC-AC converter that is phase controlled. Therefore, for it to give the required AC output voltage, it has to do a selection of the voltage input segments by applying line (natural) commutation. This explains why the output frequency is lower than the frequency input.

Harmonics in a cycloconverter are mainly affected by methods of control, overlap effect, the number of pulses in a given cycle, operation mode and mode of conduction.

There are two types of cycloconverters—

- **Step Up cycloconverter** – These types use natural commutation and give an output at higher frequency than that of the input.
- **Step Down cycloconverter** – This type uses forced commutation and results in an output with a frequency lower than that of the input.

Cycloconverters are further classified into three categories –

- **Single phase to single-phase** – This type of cycloconverter has two full wave converters connected back to back. If one converter is operating the other one is disabled, no current passes through it.
- **Three-phase to single-phase** – This cycloconverter operates in four quadrants that is $(+V, +I)$ and $(-V, -I)$ being the rectification modes and $(+V, -I)$ and $(-V, +I)$ being the inversion modes.
- **Three-phase to three-phase** – This type of cycloconverter is majorly used in AC machine systems that are operating on three phase induction and synchronous machines.

MATRIX CONVERTER

A matrix converter is defined as a converter with a single stage of conversion. It utilizes bidirectional controlled switch to achieve automatic conversion of power from AC to AC. It provides an alternative to PWM voltage rectifier (double sided). Matrix converters are characterized by sinusoidal waveforms that show the input and output switching frequencies. The bidirectional switches make it possible to have a controllable power factor input. In addition, the lack of DC links ensures it has a compact design. The downside to matrix converters is that they lack bilateral


switches that are fully controlled and able to operate at high frequencies. Its voltage ratio that is output to input voltage is limited.

There are three methods of matrix converter control –

- Space vector modulation
- Pulse width modulation
- Venturi - analysis of function transfer

The Matrix Converter Circuit

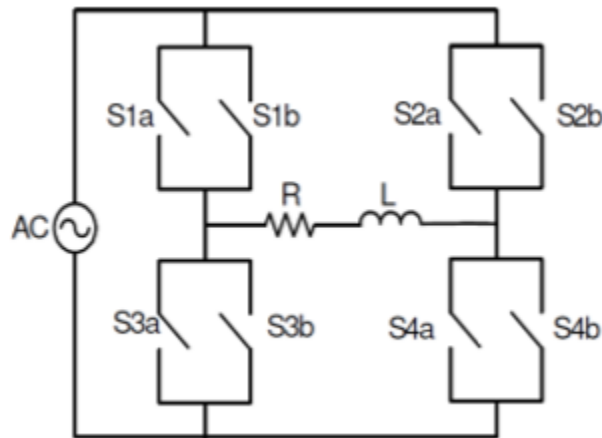The diagram given below shows a single-phase matrix converter.



It contains four bi-directional switches with each switch having the ability to conduct in both forward blocking and reverse voltage.

Space Vector Modulation (SVM)

SVM refers to a method of algorithm used to control the PWM. It creates AC waveforms that drive AC motors at various speeds. In the case of a three-phase inverter having DC supply power, its three main legs at the output are connected to a 3-phase motor.

The switches are under control to ensure that no two switches in the same leg are ON at the same time. Simultaneous ON states could result in the DC supply shorting. This leads to eight switching vectors where two are zero and six are active vectors for switching.